

tion instead of a simple resistor, because the optocouplers' nonlinear characteristic allows a higher current range without substantially affecting the noise gain of

the transimpedance amplifier. The total output noise in the circuit is 80 μV rms. A 6.8-k Ω resistor can reject the same 1.5-mA dc current, but it produces 200-

μV output noise. (DI #2364).

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 417

V/I converter accommodates grounded load

Michele Frantisek, Brno, Czech Republic

The voltage-to-current (V/I) converter in **Figure 1** uses three common op amps, two medium-power transistors, and only a few passive components. The first op amp (IC_1) inverts the sum of voltages V_{IN} and V_{OUT} to $V_1 = -(V_{\text{IN}} + V_{\text{OUT}})$. The second op amp (IC_2) and transistors Q_1 and Q_2 invert this voltage to produce $V_{\text{IN}} + V_{\text{OUT}}$. The formula for calculating the output current is thus:


$$I_{\text{OUT}} = \frac{V_2 - V_{\text{OUT}}}{R_6} = \frac{V_{\text{IN}} + V_{\text{OUT}} - V_{\text{OUT}}}{R_6} = \frac{V_{\text{IN}}}{R_6}$$

The formula shows that the value of I_{OUT} depends only on V_{IN} and R_6 . Voltage follower IC_3 reduces to a negligible level the current from the circuit output to IC_1 . The advantages of the circuit are:

- load-grounding possibility;
- simple control of $I_{\text{OUT}}/V_{\text{IN}}$ ratio;
- high precision, linearity, stability, and bandwidth;
- wide I_{OUT} range, approximately 1 μA to $I_{\text{C}}(\text{max})$ of Q_1 and Q_2 ; and
- high output resistance of approximately 50 M Ω . (DI #2365).

TO VOTE FOR THIS DESIGN,
CIRCLE NO. 418

Figure 1

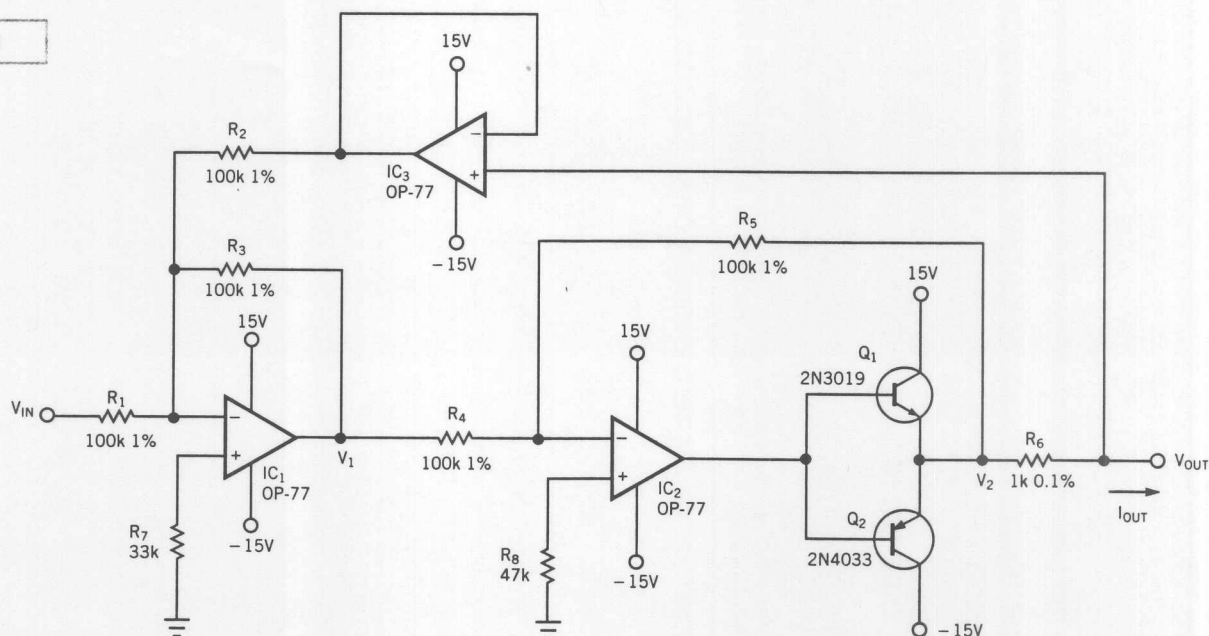

A versatile voltage-to-current converter provides a handy current source in many analog applications.